

# Tap Tempo LFO (TAPLFO V2D)

Posted May 8th, 2012 by Tom Wiltshire (<https://electricdruid.net/author/tom/>) & filed under Projects (<https://electricdruid.net/category/projects/>), Synth DIY (<https://electricdruid.net/category/synth-diy/>).

**2018 Note: Obsolete!** This chip has been superseded by the TAPLFO 3 (<https://electricdruid.net/product/taplfo3/>)

The new chip adds several features, has additional waveforms and improved resolution, and also no longer requires a crystal. It's an improvement in pretty much every way! Head over and check out the data sheet (<https://electricdruid.net/product/taplfo3/>).

This simple Tap Tempo LFO is based on the PIC 16F684. You can set the LFO frequency by tapping a tempo on a button connected to the chip, or by changing the Tempo CV. With this chip you can build tap tempo effects units or stompboxes, tap tempo controlled drum machines or tap tempo sequencer clocks. All of these are described in the datasheet below.


The LFO can produce 8 waveforms, including a random (sample & hold) wave. All the waveforms except the random wave can be altered by the wave distortion CV. See the VCLFO page (<http://www.electricdruid.com/index.php?page=projects.lfo9>) for more details of waveform distortion.



The chip also includes a tempo multiplier. This is combined with the tapped tempo to allow the LFO frequency to be set at a multiple of the tapped rate. The available multipliers are 0.5, 1, 1.5, 2, 3, and 4. This allows half- and double-time, and triplet times.

The LFO tempo, multiplier, waveform selection, wave distortion, and output level are all voltage-controlled using 0-5V. Unwanted features are easily disabled by tying the relevant pin to a constant voltage (usually 0V or +5V).

## Block Diagram

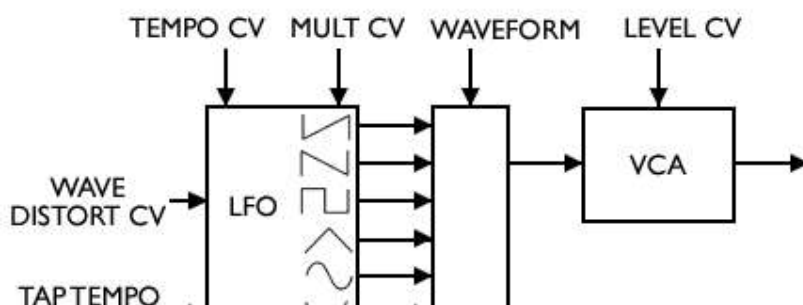

## Latest Articles




(<https://electricdruid.net/electric-druid-chips-the-next-generation/>)

Electric Druid chips: The Next Generation (<https://electricdruid.net/electric-druid-chips-the-next-generation/>)




(<https://electricdruid.net/analog-renaissance/>)

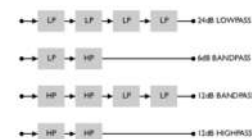Analog Renaissance? The rebirth of the impossible chips (<https://electricdruid.net/analog-renaissance/>)



(<https://electricdruid.net/multimode-filters-part-1-reconfigurable-filters/>)

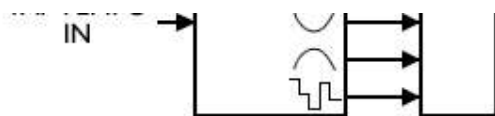
Multimode filters, Part 1: Reconfigurable



The chip uses the analogue inputs of the PIC for CVs. These are fed to the internal A/D convertor, which samples each input every 150uS or so and converts the voltage to an 8-bit value. In order to avoid using an external D/A convertor for the output, the chip uses the built-in PWM module. The PWM output needs passing through a lowpass filter to convert the pulses back into an analogue output.

Using an external crystal with the PIC allows the chip to run at its maximum clock speed of 20MHz, and this means that the PWM module is able to produce a 19.5KHz sample rate at 10-bit accuracy. Although this doesn't sound like much, in practice it is impossible to hear any artifacts in most situations.

## Pinout Diagram

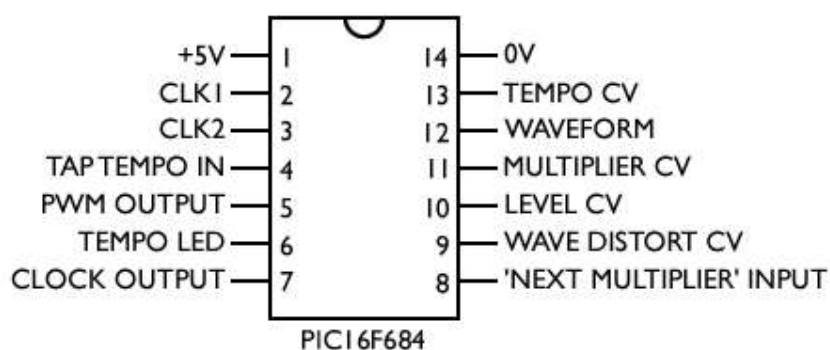

## Possible uses

The TAP TEMPO input can accept clock pulses from other equipment, which allows the LFO to be synchronised to other devices. The chip also includes a CLOCK OUTPUT which can be used to drive other equipment. This allows a tap-tempo controlled clock for an analogue sequencer or drum machine, for example.

The PWM output from the chip can be used to drive the LED in a vactrol (or similar LED/LDR combination) directly, without any subsequent op-amp filter stages. The slow response of the vactrol provides more than enough filtering. This makes for an extremely simple circuit with very few components. The vactrol's LDR can be used to replace a standard potentiometer to add tap tempo LFO control to a variety of circuits.


Example circuits are in the datasheet.

## More details

If you'd like to build one, or like to know how I built mine, perhaps you'd like to look at:

- Tap Tempo LFO PIC 16F684 ASM code (<http://www.electricdruid.net/code/TAPLFO2D.ASM>)
- Assembled HEX code from above file (<http://www.electricdruid.net>)

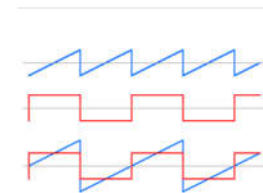filters  
(<https://electricdruid.net/multimode-filters-part-1-reconfigurable-filters/>)



(<https://electricdruid.net/a-study-of-sub-oscillators/>)

A study of Sub-Oscillators (and Oscillator Waveshaping)  
(<https://electricdruid.net/a-study-of-sub-oscillators/>)

## HOW TO BUILD A SYNTH

Our simple, powerful envelope generator, LFO, and oscillator chips can reduce the complexity of several key parts of your synth circuit. Try our projects!

## SEE ARTICLES

## BULK ORDERING

We offer price breaks for 10+ and 100+ quantities on all Electric Druid chips for manufacturers or shops. Our chips can

/code/TAPLFO2D.HEX)

- Circuit Diagram – complete modular synth tap tempo LFO (<http://www.electricdruid.net/images/lfo/TapCircuitV1.gif>)
- Circuit Diagram – tap tempo tremolo (<http://www.electricdruid.net/images/lfo/TapTremolo.gif>)
- Circuit Diagram – tap tempo sequencer clock (<http://www.electricdruid.net/images/lfo/TapClock.gif>)
- Tap Tempo LFO datasheet (includes example circuit diagrams, example waveforms, and chip pinout) (<http://www.electricdruid.net/datasheets/TAPLFO2Datasheet.pdf>)

push your product to the next level!

SEE SHOP

## The Tap Tempo LFO elsewhere on the web

There's a tap tempo tremolo project using my chip over at MusicPCB.com (<http://musicpcb.com/pcbs/tap-tempo-tremolo/>). You can get a PCB and a programmed chip for \$19. Alternatively, you can get just the chip over at Small Bear Electronics (<http://www.smallbearelec.com/servlet/Detail?no=1250>).

There has also been a lot of discussion about this project over at DIYStompboxes.com (<http://www.diystompboxes.com/smfforum/index.php?topic=76436.0>) where I initially put the idea forward. I got a lot of support, and no-one got annoyed at me for taking about nine months to finish it off! Thanks guys!

Rick Holt of Frequency Central (<http://www.frequencycentral.co.uk/>) has developed a DIY PCB for this project over at Muffwiggler.com (<http://www.muffwiggler.com/forum/viewtopic.php?t=49661>).

## Version 2

Chris Safi added the Wave Distortion feature from my original VCLFO into the TAPLFO code. I added a phase reset on the first tap to the tap tempo input. This allows you to keep the LFO on the beat with a single tap. I also tweaked some waveforms so they all reset to the top of the waveform. Finally, I used the spare pin from the first version as a digital input to step through the different multipliers. This works with the Multiplier CV in the same "either/or" way as the Tap Tempo input and the Tempo CV.

## Version 2D – a bug fix

It turns out that as a result of adding the Wave Distortion feature in version 2, it became possible for the Clock output on pin7 to drift slowly out of sync with the main LFO output. This is due to inaccuracies in the calculations building up. This is much worse at slow settings (when the increments are small, so errors are proportionally larger), and when using extreme wave distortion settings (when the errors generated are greatest). It also doesn't happen if the unit is sync'd to external pulses, since the phase is reset every time the pulses are timed.

Anyway, you're not interested in that, right? You just want to know I've fixed it, right? Right! Version 2D is the fixed version.

### FEATURED CHIP



([HTTPS://ELECTRICDRUID.NET/PRODUCT/VCDO-WAVETABLE-OSCILLATOR/](https://electricdruid.net/product/vcdo-wavetable-oscillator/))

**VCDO  
Wavetable  
oscillator**  
(<https://electricdruid.net/product/vcdo-wavetable-oscillator/>)

**£ 8**


MORE INFO  
([HTTPS://ELECTRICDRUID.NET/PRODUCT/VCDO-WAVETABLE-OSCILLATOR/](https://electricdruid.net/product/vcdo-wavetable-oscillator/))

BUY NOW  
([HTTPS://ELECTRICDRUID.NET/PRODUCT/VCDO-WAVETABLE-OSCILLATOR/?ADD-TO-CART=372](https://electricdruid.net/product/vcdo-wavetable-oscillator/?ADD-TO-CART=372))

### FEATURED CHIP
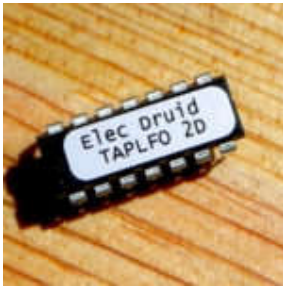
## Related Products

**TAPLFO tap tempo  
LFO**  
([https://electricdruid.net  
/product/taplfo-  
tap-tempo-lfo/](https://electricdruid.net/product/taplfo-tap-tempo-lfo/))



([https://electricdruid.net/product  
/taplfo-tap-tempo-lfo/](https://electricdruid.net/product/taplfo-tap-tempo-lfo/))


The TAPLFO chip adds a powerful feature to your LFOs: you can set the LFO frequency by tapping a tempo on a button connected to the chip, or by changing the Tempo CV. With this chip you can build tap tempo effects units or stompboxes, tap tempo controlled drum machines or tap tempo sequencer clocks. All of these are described in the datasheet below. The LFO can produce 8 waveforms, including a random (sample & hold) wave. All the waveforms...

Read more » (<https://electricdruid.net/product/taplfo-tap-tempo-lfo/>)...

More Info

([https://electricdruid.net/product  
/taplfo-tap-tempo-lfo/](https://electricdruid.net/product/taplfo-tap-tempo-lfo/)) Buy

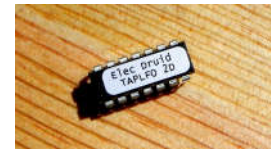21 Responses to “Tap  
Tempo LFO (TAPLFO V2D)”



([HTTPS://ELECTRICDRUID.NET  
/PRODUCT/TAPLFO-  
TAP-TEMPO-LFO/](https://ELECTRICDRUID.NET/PRODUCT/TAPLFO-TAP-TEMPO-LFO/))

**TAPLFO tap  
tempo LFO**  
([https://electricdruid.n  
/product  
/taplfo-tap-  
tempo-lfo/](https://electricdruid.net/product/taplfo-tap-tempo-lfo/))

**£ 5**

MORE INFO

([HTTPS://ELECTRICDRUID.NET  
/PRODUCT/TAPLFO-  
TAP-TEMPO-LFO/](https://ELECTRICDRUID.NET/PRODUCT/TAPLFO-TAP-TEMPO-LFO/))

BUY NOW

([HTTPS://ELECTRICDRUID.NET  
/PRODUCT/TAPLFO-  
TAP-TEMPO-  
LFO/?ADD-TO-  
CART=373](https://ELECTRICDRUID.NET/PRODUCT/TAPLFO-TAP-TEMPO-LFO/?ADD-TO-CART=373))

Now (<https://electricdruid.net/product/taplfo-tap-tempo-lfo/?add-to-cart=373>)



## ROBERT DERBY

Hi,

I have a question about the sync in/tap input on this PIC. What is the top frequency that can be input for sync'ing the chip's program to a speed? I am thinking of using this PIC to output higher frequencies in the audio range (below 880hz)

thanks

July 18th, 2016 (<https://electricdruid.net/tap-tempo-lfo-taplfo-v2d/#comment-5135>)  
Reply (<https://electricdruid.net/tap-tempo-lfo-taplfo-v2d/?replytocom=5135#respond>)



## Tom Wiltshire (<http://www.electricdruid.net/>)

Hi Robert,

I'm not sure exactly how fast it will go. I doubt it'll get as high as 880Hz though. It was \*designed\* to behave nicely up to 50Hz or so, and it does. Beyond that, I didn't test it much. What happens is that as the frequency climbs, the errors become more significant, so there's no "hard limit", just a gradual roll-off in performance.

This is for two reasons:

The frequency increment is calculated by a division, like  $1000/x$ , where  $x$  is the timing period. As  $x$  gets small, the steps between adjacent frequencies become larger, so the frequency resolution gets worse as the tap tempo period gets shorter.

The second reason is that the timing is done at the 19.5KHz sample rate, so the timing resolution is almost 1/20th msec. This is very accurate below 100Hz, but by the time you're at 1000Hz, it makes 48Hz difference – roughly 5%.

You'll also hit problems with the wave distort feature, since the calculations there assume a fairly low frequency and they don't have sufficient accuracy to go very high. That might be the limiting factor in the end.

If you give it a try, let me know!

July 21st, 2016 (<https://electricdruid.net/tap-tempo-lfo-taplfo-v2d/#comment-5174>)  
Reply (<https://electricdruid.net/tap-tempo-lfo-taplfo-v2d/?replytocom=5174#respond>)



## Shmar Mark

Hi I just ordered a couple of these chips to play with, is there a way to have the tremolo pan between two channels?

October 5th, 2016 (<https://electricdruid.net/tap-tempo-lfo-taplfo-v2d/#comment-6016>)  
Reply (<https://electricdruid.net/tap-tempo-lfo-taplfo-v2d/?replytocom=6016#respond>)



## Tom Wiltshire (<http://www.electricdruid.net/>)

You could repeat the vactrol+second op-amp part of the Tremolo circuit, and then drive the vactrol's LED from an anti-phase version of the Pin 5 PWM output. It might be possible to just use the single drive transistor and have one LED from Ground to Collector, and the other from collector to +5V, but I can't say for sure without trying it.

HTH,  
Tom

October 6th, 2016 (<https://electricdruid.net/tap-tempo-lfo-taplfo-v2d/#comment-6023>)  
Reply (<https://electricdruid.net/tap-tempo-lfo-taplfo-v2d/?replytocom=6023#respond>)



## Adam

Hi Tom. I'm breadboarding with the TapLFO right now using some of the example circuits and I have two questions:

1. I'm having trouble determining how to use both the Tap Input (with a momentary footswitch) and Tempo VR1 in the same circuit. It seems the Tap input doesn't work with the Tempo VR connected. I figured once there is a change from one of the inputs, it overrides the other? What is the correct behavior/schematic?
2. Does the Tempo LED indicate the current Tempo only when using the Tap input? It doesn't seem to output Tempo set by the Tempo VR1.

Thanks.

November 23rd, 2016 (<https://electricdruid.net/tap-tempo-lfo-taplfo-v2d/#comment-6889>)  
Reply (<https://electricdruid.net/tap-tempo-lfo-taplfo-v2d/?replytocom=6889#respond>)



## Tom Wiltshire (<http://www.electricdruid.net/>)

Reply (<https://electricdruid.net/tap-tempo-lfo-taplfo-v2d/?replytocom=6934#respond>)

Your questions tell me that you've got a fault somewhere on your breadboard! If it's working correctly, you should be able to use both the Tempo pot and the footswitch at the same time. The firmware simply uses whichever you altered last – like you said, if there's a change from one, it overrides the other. The Tempo LED should follow that latest tempo, whatever it was.

Have you got a 10K pull-up resistor on your footswitch? Is the pot properly connected between 0V and 5V? Does everything else work ok? (If not, maybe the chip's not happy at all – bad clock? Bad chip?). Drop me a line (<https://electricdruid.net/contact/>) and we'll get you debugged.

November 25th, 2016 (<https://electricdruid.net/tap-tempo-lfo-taplfo-v2d/#comment-6934>)



John Malcolm (<http://johnmalcolm.com.au>)

I would really appreciate an answer to this question about using the chip for a basic drum machine, virtually a tap-tempo metronome.

Does the output pulse start immediately with no noticeable lag? That is, is the output pulse an immediate continuation of the input pulse when the latter stops?

Thanks if you have the time to answer.

December 3rd, 2016 (<https://electricdruid.net/tap-tempo-lfo-taplfo-v2d/#comment-7068>)  
Reply (<https://electricdruid.net/tap-tempo-lfo-taplfo-v2d/?replytocom=7068#respond>)



Tom Wiltshire  
(<http://www.electricdruid.net/>)

Hi John,  
The chip times the space between two falling edges on the Tap Tempo input. That is, the input is inverted logic, or expects a short-to-ground. If you've got positive-going pulses to sync to, a transistor in front of the input is enough. There's an example in the datasheet circuits.

As soon as the chip has the new tempo, it resets itself and starts off at the new tempo.

I guess this means that if you were trying to sync it to a drum machine, you'd need one extra beat as a lead-in. So "1..1,2,3,4, etc)

If you were using it to build a drum machine, you'd be able to

tap a tempo to set the rate, but you can't stop it. Even if you  
Reply (<https://electricdruid.net/tap-tempo-lfo-taplfo-v2d/?replytocom=7108#respond>)



haven't tapped anything, it'll be running at some rate (the one set by the pot). As soon as it receives two taps, it'll jump to the new tempo.

Does that make it clearer? If you've got further questions Drop me a line (<https://electricdruid.net/contact/>) and we'll see what we can get sorted.

Tom

December 4th, 2016 (<https://electricdruid.net/tap-tempo-lfo-taplfo-v2d/#comment-7108>)



## Victor Willaredt

Hi

I am trying to make a eurorack module out of your modular lfo-circuit diagram, but I have a few questions:

How should I pull 15 volts from a eurorack to the two op amps?

How does the circuit react to for example a 12 volt external sync input?

Sorry if the answers are obvious, I am new to building circuits.

August 12th, 2017 (<https://electricdruid.net/tap-tempo-lfo-taplfo-v2d/#comment-11218>)  
Reply (<https://electricdruid.net/tap-tempo-lfo-taplfo-v2d/?replytocom=11218#respond>)




## Tom Wiltshire (<http://www.electricdruid.net/>)

You can run the circuit off the usual Eurorack supply of +/-12V instead of +/-15V. It won't matter. The only bit that is sensitive is the TAPLFO chip, and it has its own +5V supply anyway.

The External Sync input will cope with inputs up to about 20V iirc. Since I designed this circuit, I've made one modification: I recommend adding a diode. This protects the transistor if the external sync is fed with a negative-going voltage (an LFO, say). It looks like this, except this example has the TR1 and R2 the other way around. It's from the VCLFO, not the TAPLFO, so the transistor pulls the pin high instead of low – but it's the same thing.

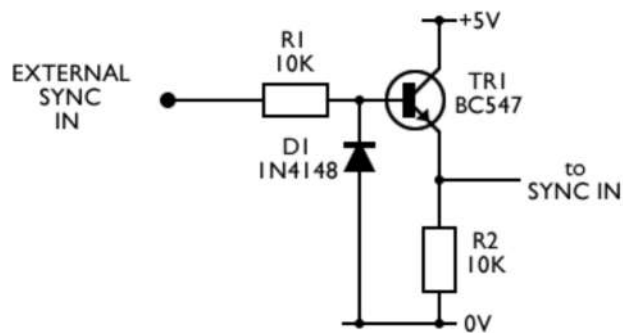Reply (<https://electricdruid.net/tap-tempo-lfo-taplfo-v2d/?replytocom=11239#respond>)





Drop me an email (<https://electricdruid.net/contact/>) if you get stuck or have any other queries.

HTH,  
Tom

August 14th, 2017 (<https://electricdruid.net/tap-tempo-lfo-taplfo-v2d/#comment-11239>)



## Andrew

Hi – I'm working on a project for my pedalboard. Will this circuit accept tap from a boss style momentary pedal, pass it through to an output, and also display the bpm speed on a small LCD?

October 13th, 2017 (<https://electricdruid.net/tap-tempo-lfo-taplfo-v2d/#comment-12575>)  
Reply (<https://electricdruid.net/tap-tempo-lfo-taplfo-v2d/?replytocom=12575#respond>)



## Tom Wiltshire (<http://www.electricdruid.net/>)

If the Boss pedal does a short-to-ground action then it could easily be connected, since that's what the tap tempo button does.

Displaying the BPM on an LCD would require some extra circuit, but I imagine such a project (Tap to LCD) exists somewhere. I think I remember doing it for a delay over on [DIYStompboxes.com](http://DIYStompboxes.com)

October 15th, 2017 (<https://electricdruid.net/tap-tempo-lfo-taplfo-v2d/#comment-12607>)  
Reply (<https://electricdruid.net/tap-tempo-lfo-taplfo-v2d/?replytocom=12607#respond>)



## Marc

Can the clock output at pin 7 be taken naked into the outside world (in a modular synth), or should it be buffered?

Reply (<https://electricdruid.net/tap-tempo-lfo-taplfo-v2d/?replytocom=13453#respond>)

November 22nd, 2017 (<https://electricdruid.net/tap-tempo-lfo-taplfo-v2d/#comment-13453>)



**Tom Wiltshire**  
(<http://www.electricdruid.net/>)

The pin can sink/source up to 25mA, so they're pretty robust, but they do need some protection. You have to judge whether you think it's worth adding extra buffers or whether you just replace a PIC worth a few pounds if you blow one up.

A worse case scenario might be -15V being connected to the output while it's high. That puts 20V across the output. A 1K resistor in series with the output would limit that to a survivable current for the PIC. That would be the most basic minimum protection that you should definitely include.

November 27th, 2017 (<https://electricdruid.net/tap-tempo-lfo-taplfo-v2d/#comment-13526>)  
Reply (<https://electricdruid.net/tap-tempo-lfo-taplfo-v2d/?replytocom=13526#respond>)



**MotorBongo** (<http://www.motorbongo.nl>)

Have a few 10-turn pots available. Would these make sense for any of the positions, or just be overkill ?

Don't know with which resolution the PIC senses the pot wipers ?

Last question: pot value not critical, right ? Saw 10kOhm stated, but I figure it's just the wiper-voltage, not its impedance, right ? (those 10-turn pots are 5 kOhm)

Thanks!

January 5th, 2018 (<https://electricdruid.net/tap-tempo-lfo-taplfo-v2d/#comment-14045>)  
Reply (<https://electricdruid.net/tap-tempo-lfo-taplfo-v2d/?replytocom=14045#respond>)



**Tom Wiltshire**  
(<http://www.electricdruid.net/>)

5K Pots will be fine. I've used values from 10K to 100K with no problems.

10 turn pots are going to cover 3600 degrees total – thats  $3600/256 = 14$  degrees per step of resolution. I guess that's not a total waste!

January 6th, 2018 (<https://electricdruid.net/tap-tempo-lfo-taplfo-v2d/#comment-14054>)  
Reply (<https://electricdruid.net/tap-tempo-lfo-taplfo-v2d/?replytocom=14054#respond>)



## MotorBongo (<http://www.motorbongo.nl>)

Thanks Tom, good to hear.

Looks then like spending 10-turn pots on 'Tempo' and possibly also 'Wave Distort' makes sense.

Thanks!

January 8th, 2018 (<https://electricdruid.net/tap-tempo-lfo-taplfo-v2d/#comment-14090>)

Reply (<https://electricdruid.net/tap-tempo-lfo-taplfo-v2d/?replytocom=14090#respond>)



## MotorBongo (<http://www.motorbongo.nl>)

Sorry for not having read the docs in full, answers part of my question already...

("8-bit resolution on the control voltages. Whether a standard potentiometer actually has the accuracy to directly produce an 8 bit resolution is another question.")

Hmm, that sounds like a nice justification to waste a 10-turn pot on! 😊

Best regards

January 5th, 2018 (<https://electricdruid.net/tap-tempo-lfo-taplfo-v2d/#comment-14046>)

Reply (<https://electricdruid.net/tap-tempo-lfo-taplfo-v2d/?replytocom=14046#respond>)



## Adam

What kind of Overvoltage protection is necessary for the CV inputs (ie speed). I want to use external voltage control for the chip. Also, What about negative voltages?

January 30th, 2018 (<https://electricdruid.net/tap-tempo-lfo-taplfo-v2d/#comment-14520>)

Reply (<https://electricdruid.net/tap-tempo-lfo-taplfo-v2d/?replytocom=14520#respond>)



## Tom Wiltshire (<http://www.electricdruid.net/>)

The recommended way is Schottky diodes from the rails to the pin. Have a look at the example schematic in the VCDO datasheet, which includes CV inputs:

<http://www.electricdruid.net/datasheets/VCDO1Datasheet.pdf>  
(<http://www.electricdruid.net/datasheets/VCDO1Datasheet.pdf>)

To be honest, when we built the Frequency Central Waverider module, we didn't include the diodes, and we didn't have any

Reply (<https://electricdruid.net/tap-tempo-lfo-taplfo-v2d/?replytocom=14528#respond>)

problems (they don't blow up). The 4K7 resistor limits current into the pin to a level the chip can handle, and it has internal protection diodes anyway, which are apparently sufficient. External diodes is a "belt and braces" approach.

To prevent negative voltages, you can add a couple of diodes to your CV input mixer to turn it into a halfwave precision rectifier, like this:

[http://www.ecircuitcenter.com/Circuits/op\\_HW\\_rectifier/Op\\_HW\\_Rectifier.htm](http://www.ecircuitcenter.com/Circuits/op_HW_rectifier/Op_HW_Rectifier.htm) ([http://www.ecircuitcenter.com/Circuits/op\\_HW\\_rectifier/Op\\_HW\\_Rectifier.htm](http://www.ecircuitcenter.com/Circuits/op_HW_rectifier/Op_HW_Rectifier.htm))

HTH,

Tom

January 31st, 2018 (<https://electricdruid.net/tap-tempo-lfo-taplfo-v2d/#comment-14528>)



Adam

Thanks

January 31st, 2018 (<https://electricdruid.net/tap-tempo-lfo-taplfo-v2d/#comment-14534>)  
Reply (<https://electricdruid.net/tap-tempo-lfo-taplfo-v2d/?replytocom=14534#respond>)

## Leave a Reply

Your email address will not be published. Required fields are marked \*

### Comment

### Name \*

### Email \*

**Website**




© 2015-2018 Electric  
Druid

All Rights Reserved.

### COMMENTS & FEEDBACK

If you've got comments, queries, or problems, please contact us (<https://electricdruid.net/contact/>). We'd love to hear your feedback about the site, our chips, and your ideas for new stuff!

### SHIPPING

Read about our shipping policy (<https://electricdruid.net/shipping/>) here.

### PERSONAL USE

Druid code and schematics are released under a CC BY-NC-SA 4.0 license (<http://creativecommons.org/licenses/by-nc-sa/4.0/>), so feel free to download and use Electric Druid code in your personal synth, pedal, or sonic blastertron 2000. Grab a copy of the schematics and tweak away to your heart's content. If you don't have a PIC programmer, you can order a chip from the shop. (/shop) Check the legal stuff (<http://www.electricdruid.net/legalstuff/>) for more details.

### COMMERCIAL USE

Electric Druid code and schematics are released under a CC BY-NC-SA 4.0 license (<http://creativecommons.org/licenses/by-nc-sa/4.0/>). Please check the legal stuff (<http://www.electricdruid.net/legalstuff/>) for more details. If you'd like to use Electric Druid chips, code, or circuits in your commercial product, we'd ask that you buy chips from us to help support the development of further projects. We can supply programmed, labelled chips in whatever quantities you need. If this isn't suitable, please

contact us (</contact>) to  
discuss your  
requirements. Thanks!